

$$\frac{R_2}{R_1 + R_2}$$

### Solution to Exercise 3.5.1

The power consumed by the resistor  $R_1$  can be expressed as

$$(v_{in} - v_{out})i_{out} = \frac{R_1}{(R_1 + R_2)^2} v_{in}^2$$

### Solution to Exercise 3.5.2

$$\frac{1}{R_1 + R_2} v_{in}^2 = \frac{R_1}{(R_1 + R_2)^2} v_{in}^2 + \frac{R_2}{(R_1 + R_2)^2} v_{in}^2$$

### Solution to Exercise 3.6.1

Replacing the current source by a voltage source does not change the fact that the voltages are identical.

Consequently,

$$v_{in} = R_2 i_{out}$$

or

$$i_{out} = \frac{v_{in}}{R_2}$$

. This result does not depend on the resistor  $R_1$ , which means that we simply have a resistor ( $R_2$ ) across a voltage source. The two-resistor circuit has no apparent use.

### Solution to Exercise 3.6.2

$$R_{eq} = \frac{R_2}{1 + \frac{R_2}{R_L}}$$

. Thus, a 10% change means that the ratio

$$\frac{R_2}{R_L}$$

must be less than 0.1. A 1% change means that

$$\frac{R_2}{R_L} < 0.01.$$

### Solution to Exercise 3.6.3

In a series combination of resistors, the current is the same in each; in a parallel combination, the voltage is the same. For a series combination, the equivalent resistance is the sum of the resistances, which will be larger than any component resistor's value; for a parallel combination, the equivalent conductance is the sum of the component conductances, which is larger than any component conductance. The equivalent resistance is therefore smaller than any component resistance.

### Solution to Exercise 3.7.1

$$v_{oc} = \frac{R_2}{R_1 + R_2} v_{in}$$

and