

## Problem 3.42: Operational Amplifiers

Find the transfer function between the source voltage(s) and the indicated output voltage for the circuits shown in Figure 3.83.

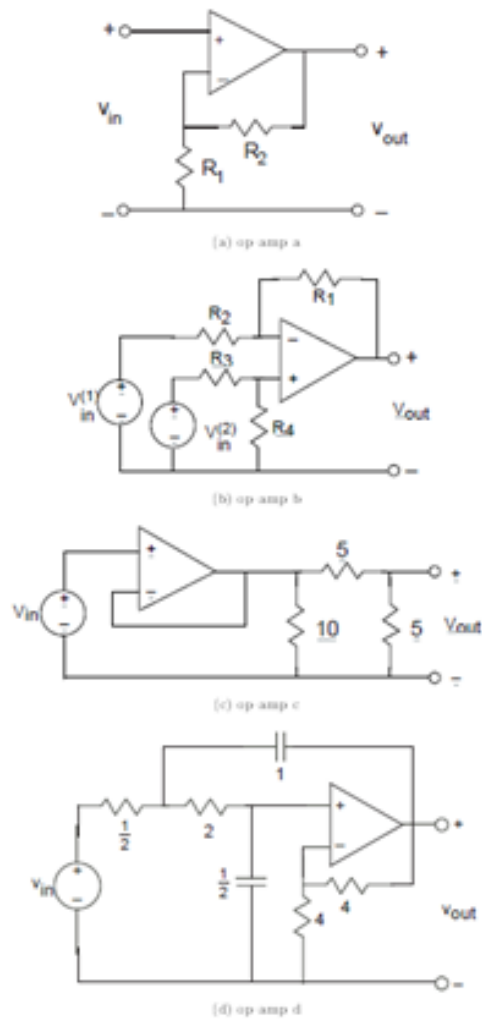


Figure 3.83 Operational Amplifiers