

Problem 3.26: More Circuit Detective Work

The left terminal pair of a two terminal-pair circuit is attached to a testing circuit. The test source $v_{in}(t)$ equals $\sin(t)$ (Figure 3.69).

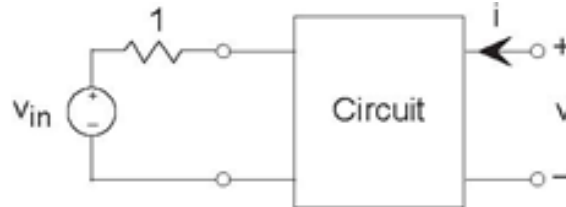


Figure 3.69 More Circuit Detective Work

We make the following measurements.

- With nothing attached to the terminals on the right, the voltage $v(t)$ equals

$$\frac{1}{\sqrt{2}} \cos\left(t + \frac{\pi}{4}\right)$$

.

- When a wire is placed across the terminals on the right, the current $i(t)$ was $-(\sin(t))$.
1. What is the impedance "seen" from the terminals on the right?
 2. Find the voltage $v(t)$ if a current source is attached to the terminals on the right so that $i(t) = \sin(t)$.